

**Design and Implementation of a
Coin-Operated Vending Machine Using Verilog**

Samuel Singaram

CONTENTS

1.	Introduction.....	01
2.	State Diagram.....	01
3.	States transitions.....	02
4.	About Language used.....	02
5.	Verilog Design Code.....	03
6.	Test Bench Code.....	06
7.	Results.....	09
8.	References.....	10


1. Introduction

The vending machine is a finite state machine (FSM) designed to dispense a product upon receiving the appropriate payment. This project simulates a vending machine with three states, accepting ₹5 and ₹10 coins, while calculating the total payment and returning change if needed. The machine is implemented using Verilog and tested using a Verilog test bench.

 2. State Diagram

The vending machine operates in three states:

- **S0 (Initial State):** No coins inserted.
- **S1:** ₹5 has been inserted.
- **S2:** ₹10 has been inserted.



Each state transition depends on the input coin value (₹0, ₹5, or ₹10) and the cumulative amount.

3. State Transitions

The state transitions are as follows:

- From **S0**:
 - ₹5 → Move to **S1**.
 - ₹10 → Move to **S2**.
- From **S1**:
 - ₹5 → Move to **S2**.
 - ₹10 → Dispense product and return to **S0**.
- From **S2**:
 - ₹5 → Dispense product and return to **S0**.
 - ₹10 → Dispense product, return ₹5 as change, and move to **S0**.

The default behavior ensures the FSM resets to **S0** on invalid inputs or a reset signal.

4. About Language Used

The vending machine project is implemented using **Verilog HDL (Hardware Description Language)**, a popular language for designing and simulating digital circuits. Verilog provides a concise and flexible framework for defining hardware behavior, enabling the modeling of combinational and sequential logic with ease.

Key Features of Verilog:

Structural and Behavioral Modeling:

Verilog supports both low-level structural descriptions and high-level behavioral descriptions, making it suitable for a wide range of applications.

Event-Driven Simulation:

Verilog uses an event-driven simulation model, allowing for the precise analysis of circuit behavior over time.

Concurrency:

It allows concurrent execution of statements, reflecting real-world hardware behavior where multiple components operate simultaneously.

Parameterized Designs:

Verilog allows parameterization, making designs more reusable and scalable.

5. Verilog Design Code

```
module vending_machine(  
  
    input clk,  
  
    input reset,  
  
    input [1:0]in, //input 2'b0=0rs, 2'b01=5rs 2'b10=10rs  
  
    output reg out, //dispenses product  
  
    output reg [1:0]change, //returns change or balance amount  
  
    output reg [1:0]c_state,n_state  
  
    );  
  
    parameter s0=2'b00;  
  
    parameter s1=2'b01;  
  
    parameter s2=2'b10;  
  
  
    always@(posedge clk)  
  
    begin  
  
        if(reset)  
  
            begin  
  
                c_state=0;  
  
                n_state=0;  
  
                change=2'b00;  
  
            end  
  
        else
```

```

c_state=n_state;

case(c_state)
s0:
if(in==2'b00)
begin
n_state=0;
out=0;
change=2'b00;
end
else if(in==2'b01)
begin
n_state=1;
out=0;
change=2'b00;
end
else if(in==2'b10)
begin
n_state=2;
out=0;
change=2'b00;
end
s1:
if(in==2'b00)
begin

```

```

        n_state=0;

        out=0;

        change=2'b01;
    end
else if(in==2'b01)
    begin
        n_state=2;

        out=0;

        change=2'b00;
    end
else if(in==2'b10)
    begin
        n_state=0;

        out=1;

        change=2'b00;
    end
end
s2:
if(in==2'b00)
    begin
        n_state=0;

        out=0;

        change=2'b10;
    end
else if(in==2'b01)
    begin

```

```

        n_state=0;

        out=1;

        change=2'b00;

    end

    else if(in==2'b10)

    begin

        n_state=0;

        out=1;

        change=2'b01;

    end

    //default: c_state=s0;

endcase

end

endmodule

```

6. Test Bench Code

```

module vending_machine_tb;

```

```

    // Inputs

```

```

    reg clk;

```

```

    reg reset;

```

```

    reg [1:0] in;

```

```

    // Outputs

```



```

wire out;

wire [1:0] change;

wire [1:0] c_state;

wire [1:0] n_state;


// Instantiate the Unit Under Test (UUT)

vending_machine uut (

    .clk(clk),

    .reset(reset),

    .in(in),

    .out(out),

    .change(change),

    .c_state(c_state),

    .n_state(n_state)

);


initial begin

    clk = 0;

    reset = 1;

    // Test Case 1: Insert ₹5, ₹5, ₹5

    #6 reset=0;

    in = 2'b01; // ₹5

    #11 in=2'b01; // ₹5

    #16 in=2'b01; // ₹5

```

```
/* Test Case 2: Insert ₹5, ₹10
```

```
    #6 reset=0;
```

```
    in = 2'b01; // ₹5
```

```
    #11 in=2'b10; // ₹10 */
```

```
/* Test Case 3: Insert ₹10, ₹10
```

```
    #6 reset=0;
```

```
    in = 2'b10; // ₹10
```

```
    #11 in=2'b10; // ₹10 */
```

```
/* Test Case 4: Insert ₹5, then nothing
```

```
    #6 reset=0;
```

```
    in = 2'b01; // ₹5 */
```

```
/* Test Case 5: Insert ₹10, then nothing
```

```
    #6 reset=0;
```

```
    in = 2'b10; // ₹10 */
```

```
#11 $finish;
```

```
    end
```

```
    initial begin
```

```
        $dumpfile("vending_machine.vcd");
```

```
        $dumpvars(1,vending_machine_tb);
```


```
forever #5 clk=~clk;
```

```
end
```


```
Endmodule
```

7. Results


1.Adding 5 Rs three times consecutively

 


2.Adding 5 Rs and then 10 Rs

 


3.Adding 10 Rs two times

 

4.Adding 5 Rs and then nothing

 

5.Adding 10 Rs and then nothing

 

8. References

- Samir Palnitkar, *"Verilog HDL: A Guide to Digital Design and Synthesis."*
- IEEE Standard for Verilog Hardware Description Language.
- Online resources on FSM design and Verilog simulation(youtube etc..).